

ENGR 2323 Digital Design Lab

Lab 3 Realizing Combinational Circuits using Discrete Logic

Fall 2022 Lab 3 Function Table

U	V	W	X	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

Figure 1. Function Table for Lab 3

References

None

Last modified Thursday, August 18, 2022



This work is licensed under a [Creative Commons Attribution-NonCommercial-ShareAlike 4.0 International License](https://creativecommons.org/licenses/by-nc-sa/4.0/).